 


# Intro to Computer Logic – Part I




CPSC 240-09  
John Overton

# Section Outline

- Boolean Algebra and Logic Design
- Simplification of Boolean Functions using K-maps
- Combinatorial Circuits (decoders and multiplexors )
- Sequential Circuits (Flip-Flops, latches)
- Look at two other computer architectures: The ATmega and ARM Cortex M
 
# Binary Addition

- Starting with the LSB, add each pair of digits, include the carry if present.



# Forming the Two's Complement

- Negative numbers are stored in two's complement notation
- Represents the **additive Inverse**

Starting value	00000001
Step 1: reverse the bits	11111110
Step 2: add 1 to the value from Step 1	11111110 +00000001
Sum: two's complement representation	11111111

# Binary Subtraction

- When subtracting  $A - B$ , convert  $B$  to its two's complement
- Add  $A$  to  $(-B)$

$$\begin{array}{r} 00001100 \\ -00000011 \\ \hline \end{array} \longrightarrow \begin{array}{r} 00001100 \\ +11111101 \\ \hline 00001001 \end{array}$$

Practice: Subtract 0101 from 1001.

# Boolean Operations

- NOT  $\neg$ , the overbar, ' (prime)
- AND  $\wedge$  (cap),  $\cdot$
- OR  $\vee$  (cup),  $+$
- Operator Precedence
- Truth Tables

# Boolean Algebra

- Based on **symbolic logic**, designed by George Boole
- Boolean expressions created from:
  - NOT, AND, OR

Expression	Description
$\neg X$	NOT X
$X \wedge Y$	X AND Y
$X \vee Y$	X OR Y
$\neg X \vee Y$	( NOT X ) OR Y
$\neg (X \wedge Y)$	NOT ( X AND Y )
$X \wedge \neg Y$	X AND ( NOT Y )

# Operator Precedence

- Examples showing the order of operations:

Expression	Order of Operations
$\neg X \vee Y$	NOT, then OR
$\neg(X \vee Y)$	OR, then NOT
$X \vee (Y \wedge Z)$	AND, then OR



# Truth Tables (1 of 3)

- A **Boolean function** has one or more Boolean inputs, and returns a single Boolean output.
- A **truth table** shows all the inputs and outputs of a Boolean function

Example:  $\neg X \vee Y$

X	$\neg X$	Y	$\neg X \vee Y$
F	T	F	T
F	T	T	T
T	F	F	F
T	F	T	T

# Truth Tables (2 of 3)


- Example:  $X \wedge \neg Y$

$X$	$Y$	$\neg Y$	$X \wedge \neg Y$
F	F	T	F
F	T	F	F
T	F	T	T
T	T	F	F

# Truth Tables (3 of 3)

- Example:  $(Y \wedge S) \vee (X \wedge \neg S)$

X	Y	S	$Y \wedge S$	$\neg S$	$X \wedge \neg S$	$(Y \wedge S) \vee (X \wedge \neg S)$
F	F	F	F	T	F	F
F	T	F	F	T	F	F
T	F	F	F	T	T	T
T	T	F	F	T	T	T
F	F	T	F	F	F	F
F	T	T	T	F	F	T
T	F	T	F	F	F	F
T	T	T	T	F	F	T

 

Two-input multiplexer

# TTL Circuits

- Towards the 60's, common logic circuits were packages manufactured by Motorola, Texas Instruments, Fairchild and other manufacturers
- These devices packaged different gates in different combinations with the thought that they could be combined to create many different types of digital products (such as computers)
- These devices are still manufactured today, but not in the quantities manufactured through the 80's.
- However, they are still needed and used in many digital products (such as computers or computing systems)
- We will look at a few 5 volt TTL parts (from the 74LSnn series).
- Modern computer chips run at lower voltages (3.3 volts, 1.8 volts, etc.)  
There are newer TTL parts that run at lower voltages


# Programmable Gate Arrays

- Programmable logic devices are devices that can be programmed to take on the functionality of millions of gates – PLDs (PAL, GAL, CPLD), Field Programmable gate arrays (FPGA).
- Usually these programmable gate arrays are programmed using a language such as Verilog or VHDL
- Cell libraries and IP libraries can be purchased that will assist in creating a larger system on an FPGA chip

# NOT

- Inverts (reverses) a boolean value
- Truth table for Boolean NOT operator:


$X$	$\neg X$
F	T
T	F

 

# AND

- Truth table for Boolean AND operator:


<b>X</b>	<b>Y</b>	<b><math>X \wedge Y</math></b>
F	F	F
F	T	F
T	F	F
T	T	T

 

# OR

- Truth table for Boolean OR operator:

X	Y	$X \vee Y$
F	F	F
F	T	T
T	F	T
T	T	T

 




# Exclusive OR


- Truth table for Boolean XOR operator:

Input		Output
A	B	O
0	0	0
0	1	1
1	0	1
1	1	0

 


# Building an Adder

Input		Output	
A	B	O	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

# Building an Adder

Input		Output	
A	B	O	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

# Building an Adder


Input			Output	
<u>Cin</u>	A	B	O	<u>Cout</u>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

If we can build a full adder for one bit, then we can chain as many together as we need (for example 8 for 8-bit addition, 32 for 32-bit addition or even 64 for 64-bit addition)

# Building an Adder


Input			Output	
<u>Cin</u>	A	B	O	<u>Cout</u>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 The black lines in the schematic on the left are from the original half-adder. The red lines and components are added to make a full adder.



 
# Building an Adder

- Here's another view of the full adder – it is actually two half adders put together plus an additional OR gate for Cout



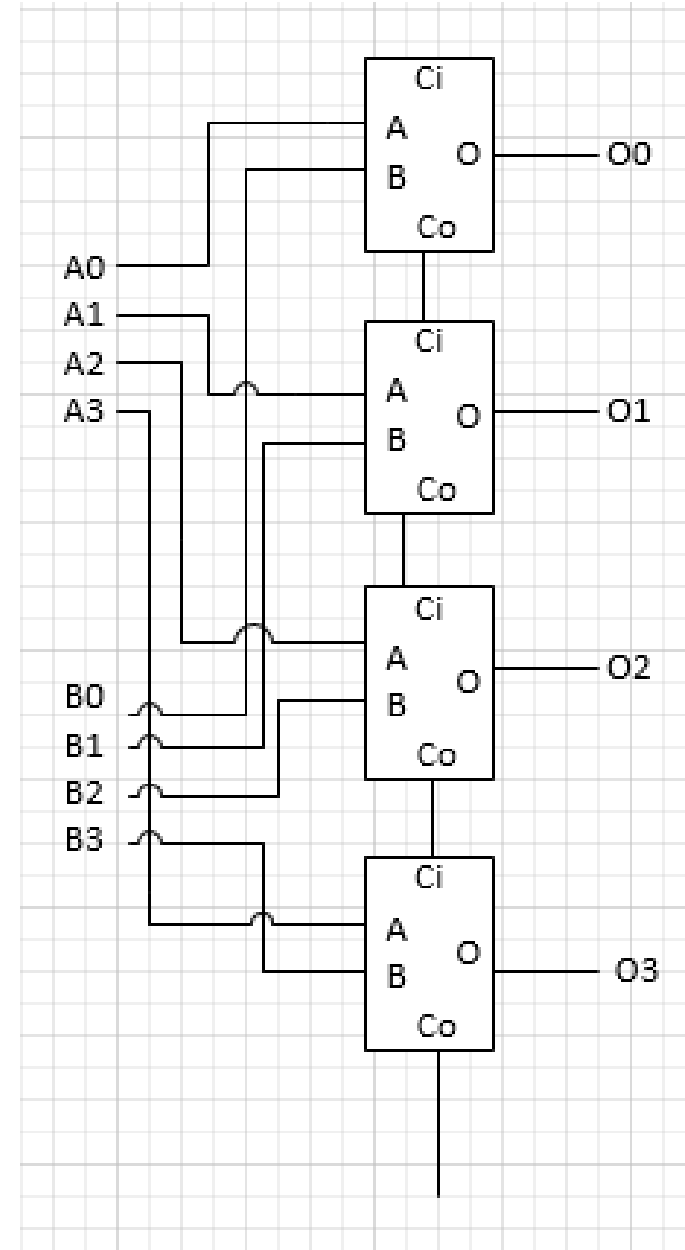
# Combining 1-bit adders

- We can combine 1-bit adders to get the number of bits that we need


 
# Building a computer

<https://www.youtube.com/watch?v=HyznrdDSSGM&list=PLOWKtXNTBypGqImE405J2565dvjafglHU>





<https://simulator.io/>

simulator

Anonymous board

Unsaved changes. Click [Link](#) or [Fork](#) to save.

LoginRegister

RUN

Aa

Elements

GATES

&

$\geq 1$

=1

1•

1

BASIC

0

CLK

ADDER

HA

FA

Options

No options available for this tool/element

<https://circuitverse.org/simulator>

