
Decoders

A circuit that changes a code into a set of signals and does the opposite job of an *encoder*.

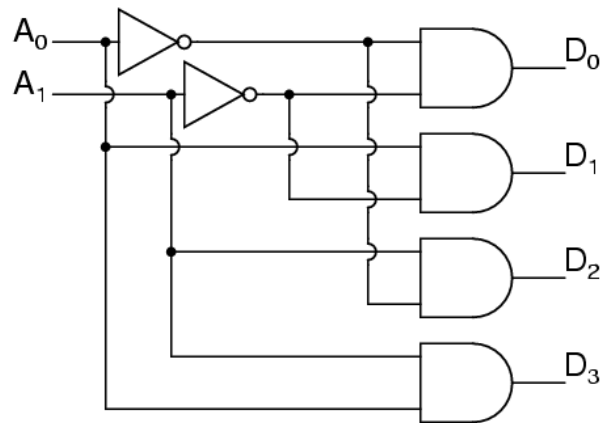


Figure 1: Decoder Example