 


# Intro to Computer Logic – Part III




CPSC 240-09  
John Overton

# Sequential circuits: Flip-Flops.

- Flip-flops are 1 bit circuit that has two stable states
- Generally, there are 4 varieties: SR, D, JK and T
- Flip-flops can be either simple (latched) or clocked
- Clocked flip-flops ignore their inputs until the clock signal is toggled:
  - Some clocked flip-flops change state on the rising edge of the clock signal
  - Other clocked flip-flops change state on the falling edge of the clock signal
- Flip-flops are subject to a problem called metastability – when clock and data change at about the same time and the order is not clear. Not usually a problem because hardware designers follow the flip-flop's timing specifications when using these parts in their designs
 
# The SR Flip-Flop (latch)

- When S and R are low, the outputs Q and Q' are in a constant state.
- Q and Q' are complementary. When Q is high, Q' is low and vice-versa.
- If S is pulsed high when R is low, then Q goes high and stays high even when S returns to low.
- If R is pulsed high while S is held low, then Q goes low and stays low even when R returns to low.




# The D Latch

- When E is high, Q follows D with Q' the complement of Q
- When E is low, the output remains the same (no state change) and D is ignored

E – Enable

D – Data

Q Q' - Output

 

**Gated D latch truth table**

E/C	D		Q	$\overline{Q}$	Comment
0	X		$Q_{prev}$	$\overline{Q}_{prev}$	No change
1	0		0	1	Reset
1	1		1	0	Set

# The D Flip-flop (clocked)

- The D flip-flop captures the value of the D input at a specific portion of the clock cycle – either the rising edge or the falling edge

> – Clock


D – Data

Q Q' – Output

S – Set

R – Reset

 What is a clock cycle? It is the clock line going high and then low again. A rising edge is the portion when the clock line goes from low-to-high. The falling edge is the clock line going from high-to-low.




Clock	D	Q <sub>next</sub>
Rising edge	0	0
Rising edge	1	1
Non-Rising	X	Q

The S (set) and R (reset) inputs can be used to immediately change state

Inputs				Outputs	
S	R	D	>	Q	Q'
0	1	X	X	0	1
1	0	X	X	1	0
1	1	X	X	1	1
 
# JK Flip-Flop


- The JK flip-flop is similar to the SR latch where J is similar to the Set input and K is similar to the Reset input.
- However, all state changes are synced to a clock input: When J is high and K is low, on the next clock rising edge, Q will go high. When K is high and J is low, on the next clock rising edge Q will go low.
- When both J and K are low, no state change happens during clock cycles
- However, an interesting case happens when both J and K are high: In this case, on the rising clock edge, no matter what state Q was in, it will change to the opposite state – it will flip.



J	K	Clock	Comment	Q <sub>next</sub>
0	0	Rising	Hold state	Q
0	1	Rising	Reset	0
1	0	Rising	Set	1
1	1	Rising	toggle	Q'

 
# T Flip-flop

- When T is high, every clock cycle will toggle the outputs



T	Q	Clock	Comment	Qnext
0	0	Rising	Hold state	0
0	1	Rising	Hold state	1
1	0	Rising	Toggle	Q' (1)
1	1	Rising	Toggle	Q' (0)

Example using shift registers

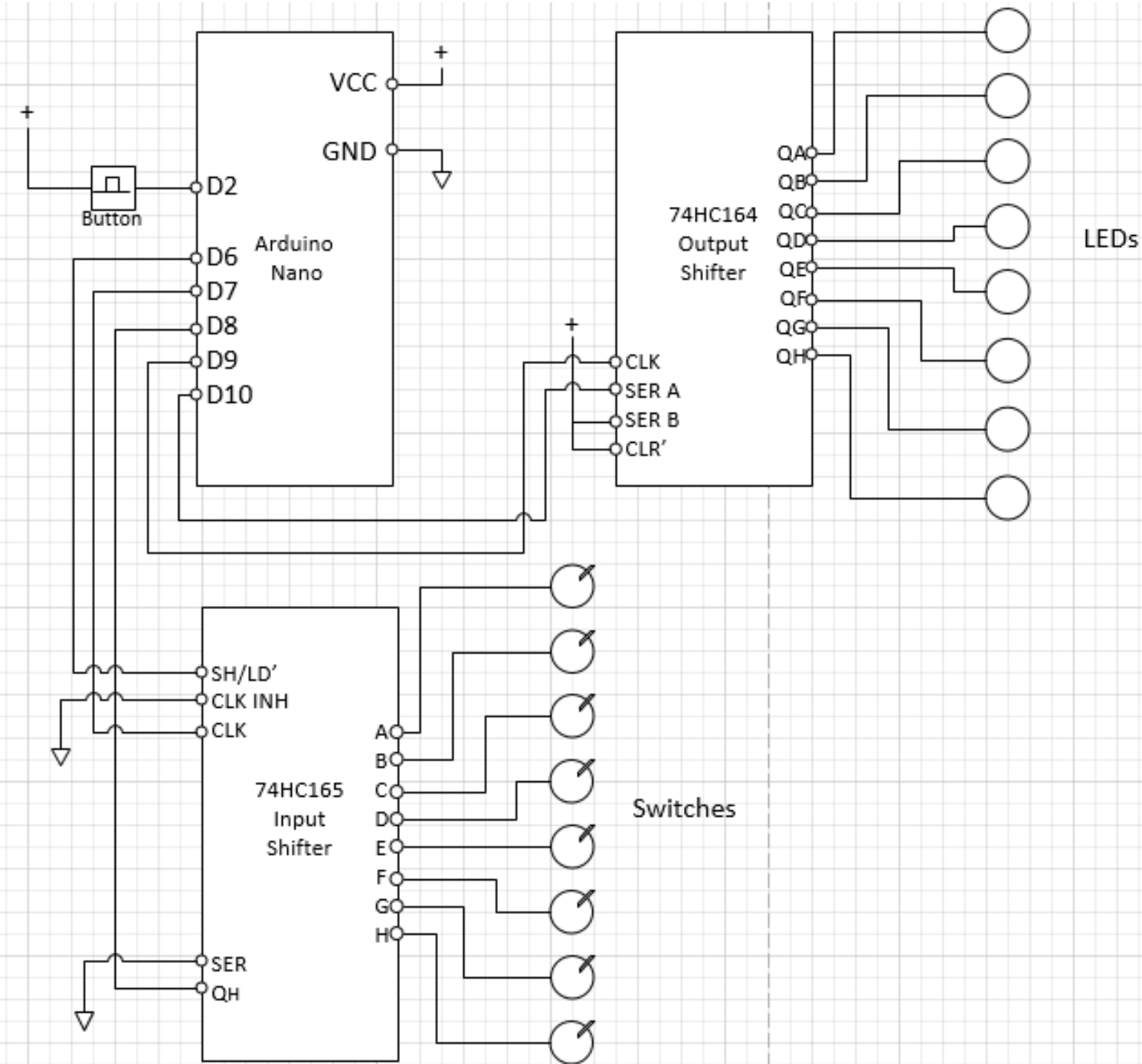



# Decoders

# Assignment

- Use one of the online simulators to see how various flip-flops work:
  1. Build an 3 x 8 output decoder
  2. Build a shift register used as an output

Upload your work as screen shots.

simulator

Anonymous board

Unsaved changes. Click [Link](#) or [Fork](#) to save.

LoginRegister

RUN

Aa

▼ Elements

GATES

&

≥1

=1

1•

1

BASIC

0

■

●

CLK →

ADDER

HA

FA

▼ Options

No options available for this tool/element

```
graph LR; I1[0] --- J1(( )); I2[0] --- J2(( )); J1 --- O1[=1]; J2 --- O2[&]; O1 --- T1(( )); O2 --- T2(( ))
```

<https://circuitverse.org/simulator>

